

VLSI LAB ASSIGNMENT

Encoder

1. Design a 4x2 Encoder using
 - (a) structural modelling.
 - (b) using behavioral modelling.
2. Design a 8x3 Encoder using
 - (a) select statement.
 - (b) case statement.
3. Design a decimal-to-BCD encoder.

Multiplexer

4. Design a 2x1 Multiplexer by
 - (a) structural modelling.
 - (b) process statement (using case statement and if else statement).
 - (c) concurrent statement.
5. Design a 4x1 Multiplexer by
 - (a) structural modelling.
 - (b) process statement (using case statement and if else statement).
 - (c) concurrent statement.
 - (d) by component instantiation.
6. Design a 8x1 Multiplexer by
 - (a) using only 2x1 Multiplexers.
 - (b) using both 2x1 Multiplexers and 4x1 Multiplexers.
7. Design a 16x1 Multiplexer using component instantiation.

Decoder

8. Design 1x2 Decoder using
 - (a) structural design.
 - (b) sequential statement.
 - (c) concurrent statement.
9. Design 2x4 Decoder using
 - (a) structural design.
 - (b) sequential statement.
 - (c) concurrent statement.

10. Design a 3x8 decoder
 - (a) by component instantiate.
 - (b) by using procedural statement.

Demultiplexer

13. Design a 1x2 Demultiplexer and 1x4 Demultiplexer using structural design and behavioral design.
12. Design a 1x16 Demultiplexer
 - (a) using only 1x4 Demultiplexers.
 - (b) using only 1x2 Demultiplexers.
 - (c) using only and both 1x2 Demultiplexers and 1x8 Demultiplexers.
 - (d) using only and both 1x2 Demultiplexers and 1x4 Demultiplexers.

ADDER

14. Design Half Adder using gate level modelling.
15. Design Full Adder using
 - (a) component instantiate.
 - (b) using function or procedure.
16. Design 4-bit Ripple-Carry-Adder by
 - (a) using generate statement.
 - (b) using Loop statement.
17. Design BCD Adder.
18. Design Adder/Subtractor circuit.

Flip-Flop

19. Design SR Flipflop.
20. Design D Flipflop.
21. Design JK Flipflop.
22. Design T Flipflop.

Counter

23. Design a 4-bit synchronous Counter using JK Flipflop.