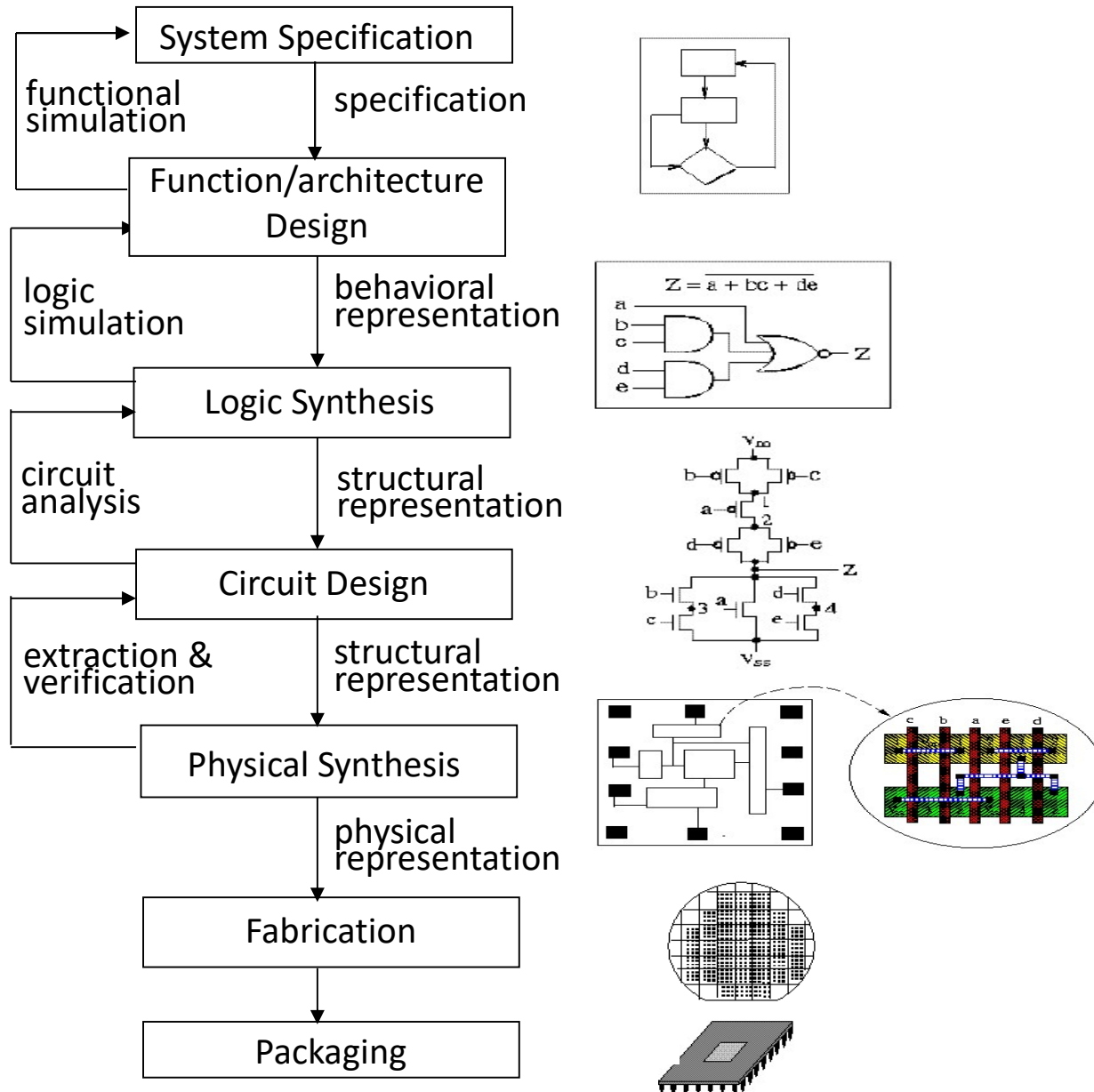


Logic Design by MOS Gates

VLSI Design Flow




Conduction Complement

- Complementary CMOS gates always produce 0 or 1

- Ex: NAND gate

 - Series nMOS: $Y=0$ when both inputs are 1
- Thus $Y=1$ when either input is 0
- Requires parallel pMOS




- Rule of *Conduction Complements*

- Pull-up network is **complement** of pull-down
- Parallel \rightarrow series, series \rightarrow parallel



Realization by NAND Gates

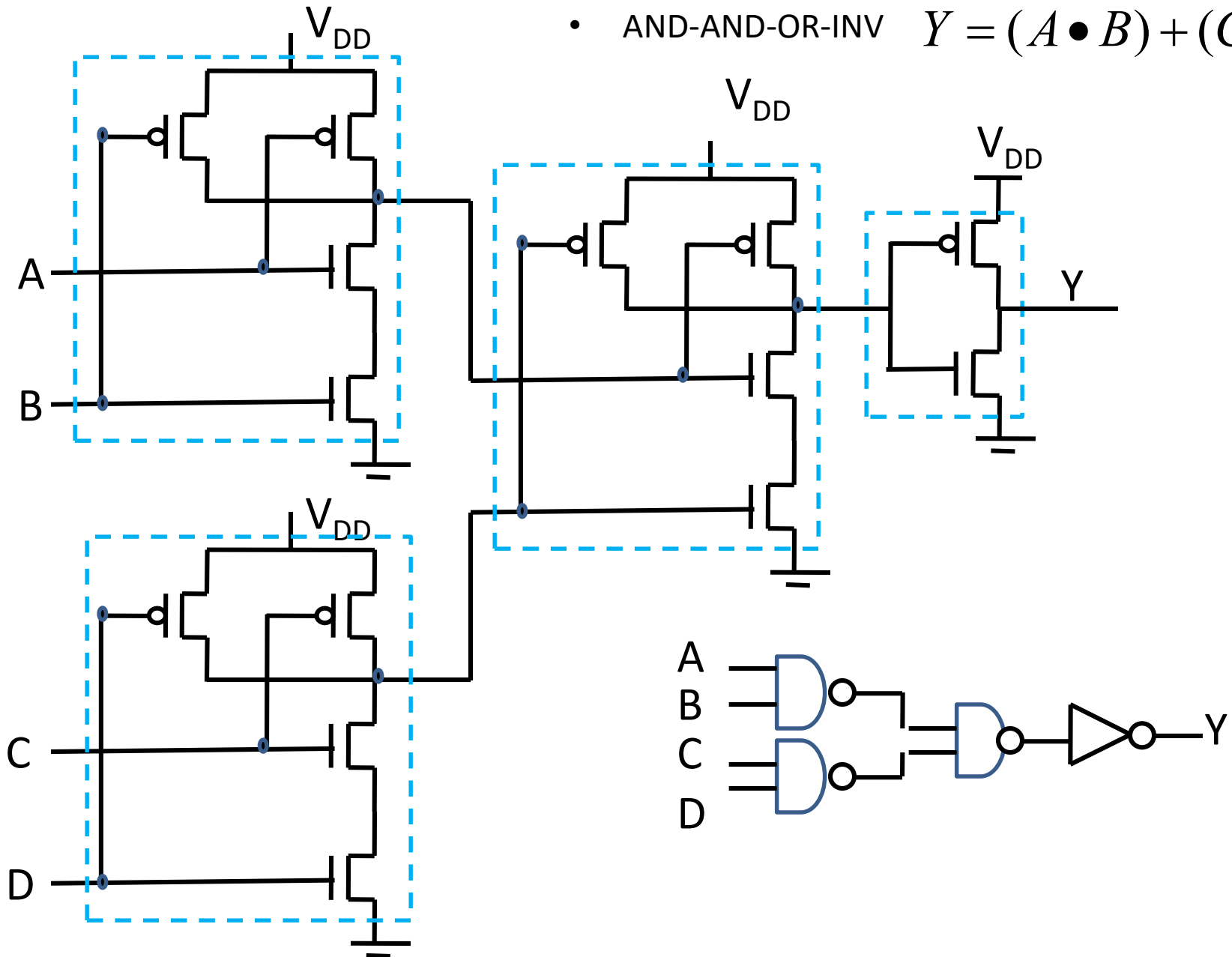- AND-AND-OR-INV $Y = \overline{(A \bullet B) + (C \bullet D)}$




CMOS Gate Design

- CMOS NOR gate

  


Realization by NOR Gates

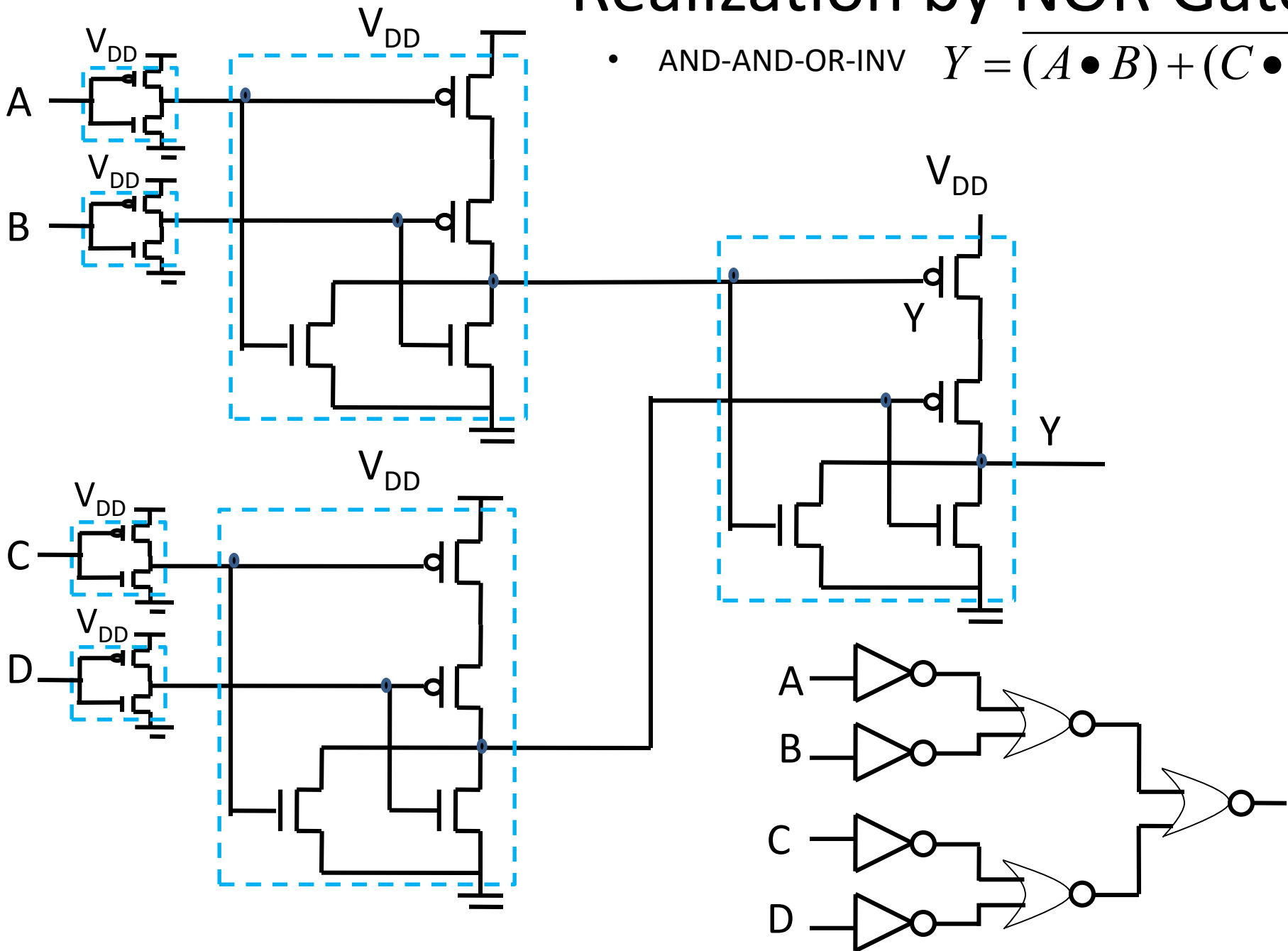- AND-AND-OR-INV $Y = \overline{(A \bullet B) + (C \bullet D)}$




Complementary CMOS (single complex cell)

 - Complementary CMOS logic gates
 - nMOS *pull-down network*
 - pMOS *pull-up network*
 - a.k.a. static CMOS





	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)


Series and Parallel

 


(a)

  



(b)

 

 
- nMOS: 1 = ON
- pMOS: 0 = ON
- *Series*: both must be ON
- *Parallel*: either can be ON



(c)

  


(d)

 

Compound Gates


Compound gates can do any inverting function
 
$$\bullet Y = \overline{(A + B + C) \bullet D}$$



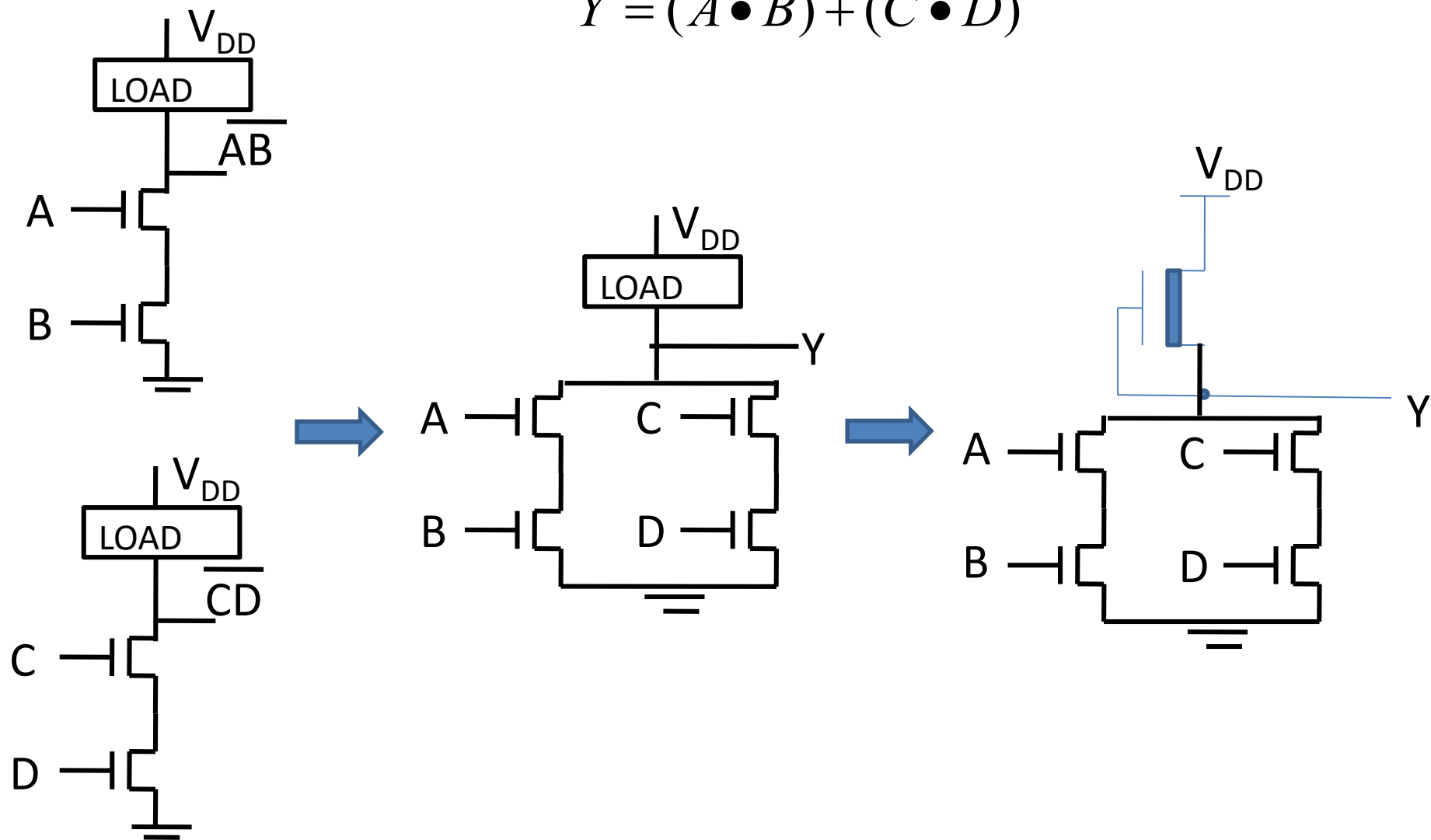
Example:


$$Y = \overline{(A \bullet B) + (C \bullet D)}$$



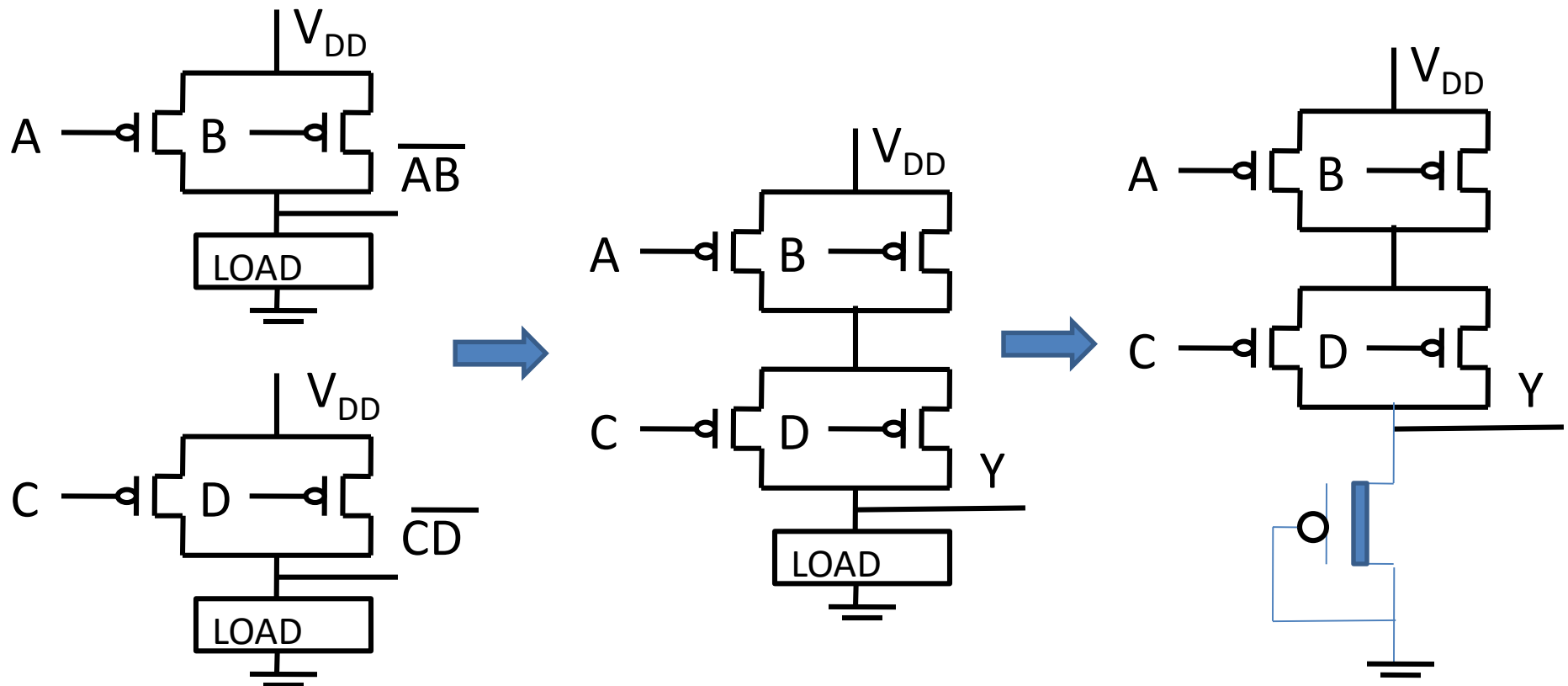Example:



$$Y = \overline{(A \bullet B) + (C \bullet D)}$$



 

  
Example:

$$Y = \overline{(A \bullet B) + (C \bullet D)}$$




Several Realizations: NMOS
 
$$Y = \overline{AB + CD} = \overline{\overline{\overline{AB + CD}}} = \overline{\overline{\overline{(A+B)(C+D)}}} = \overline{\overline{\overline{A} \overline{C} + \overline{B} \overline{C} + \overline{A} \overline{D} + \overline{B} \overline{D}}} = \overline{(\overline{A} + \overline{C})(\overline{B} + \overline{C})(\overline{A} + \overline{D})(\overline{B} + \overline{D})}$$




Series-Parallel (SP)

 


Parallel-Series (PS)

Several Realizations: PMOS
 
$$Y = \overline{AB + CD} = (\overline{A+B})(\overline{C+D}) = \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}\overline{D} + \overline{B}\overline{D}$$





Parallel-Series (PS)

 


Series-Parallel (SP)

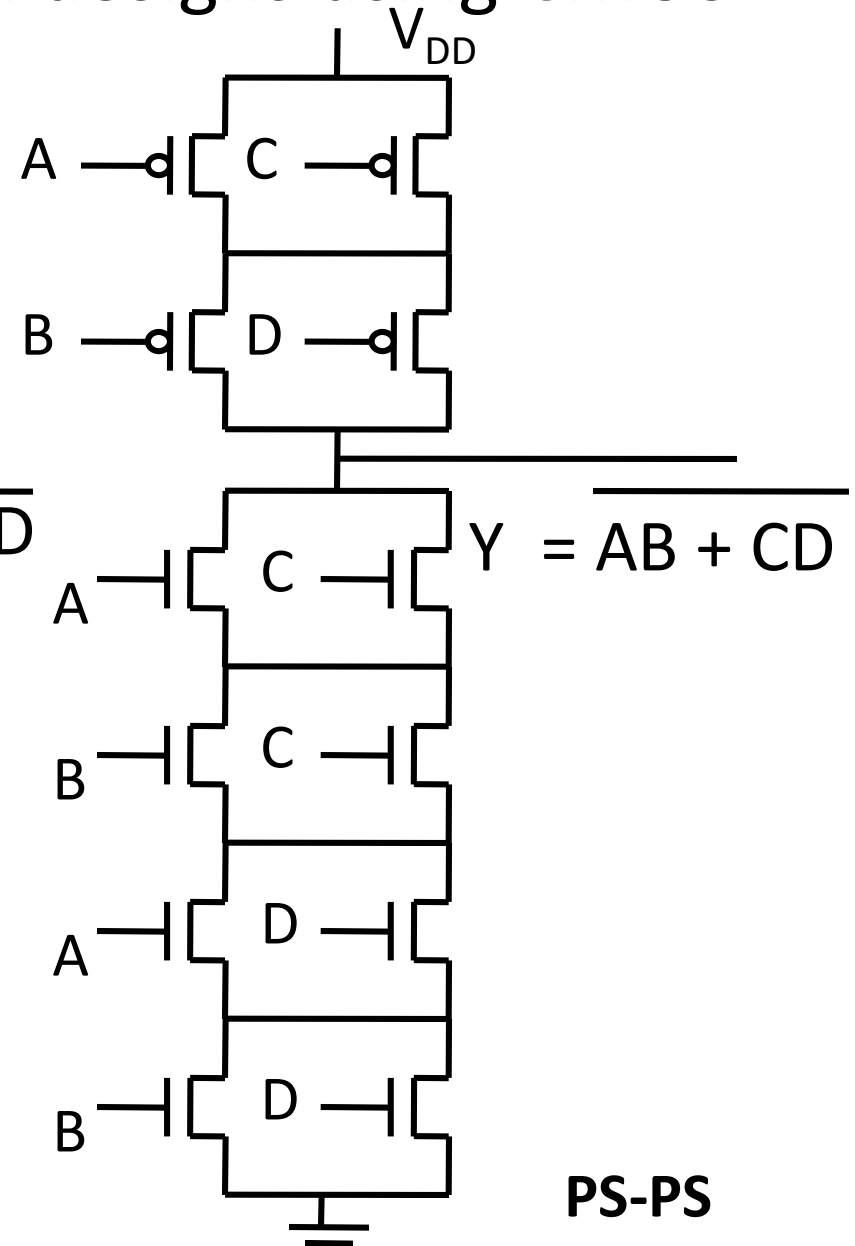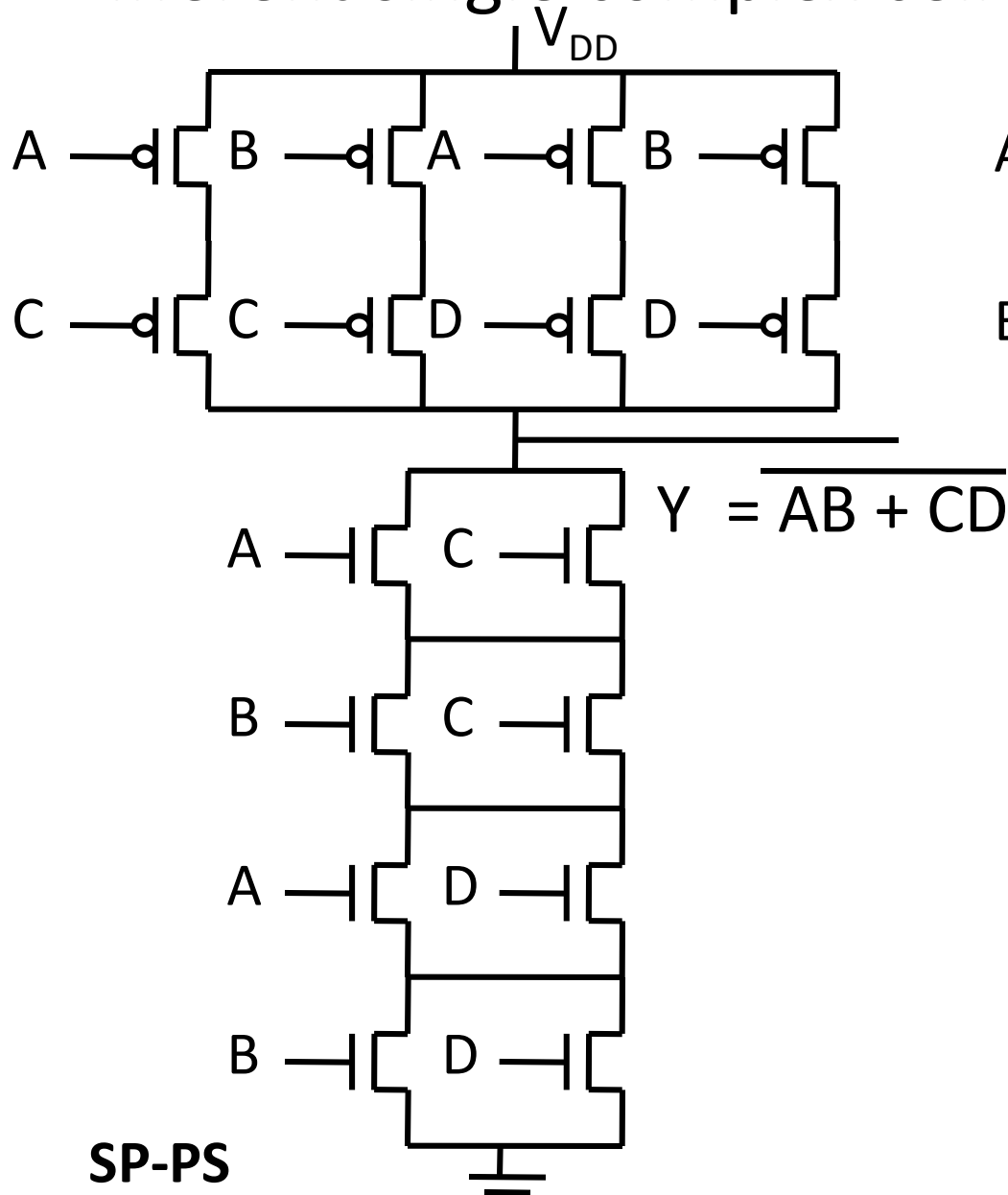
Different single complex cell designs using CMOS



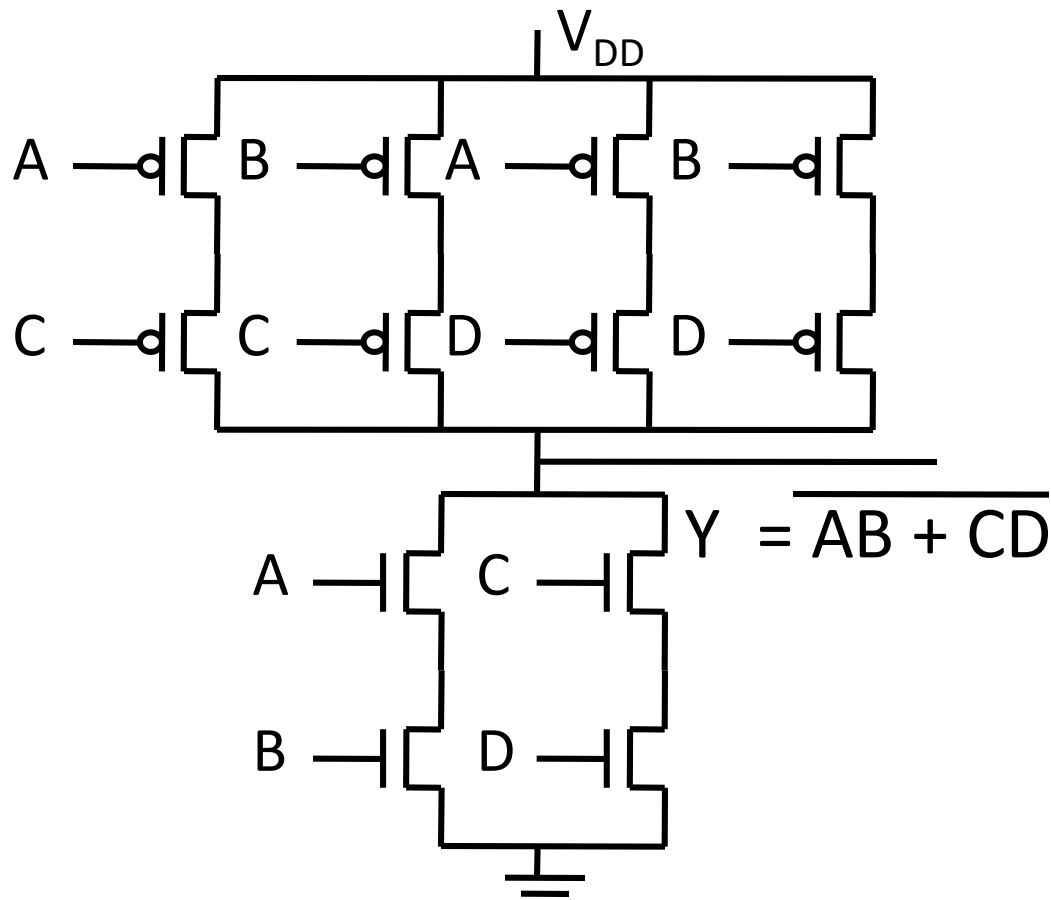Different single complex cell designs using CMOS



SP-SP

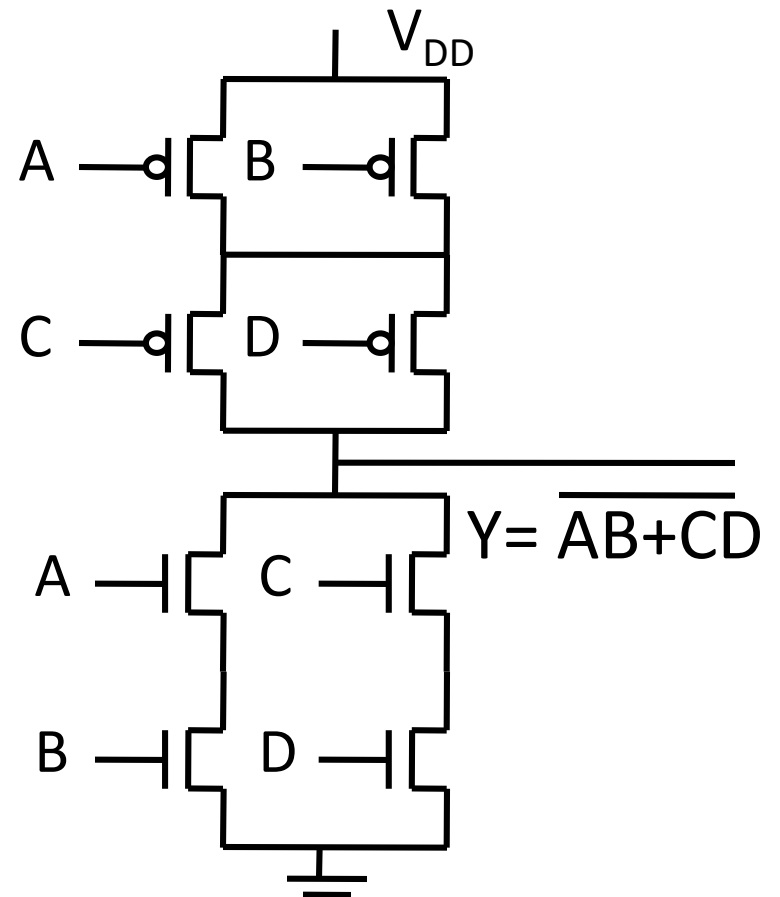


PS-SP

•

$$Y = \overline{(AD + BD + CD)}$$

- $Y = \overline{(AD + BD + CD)}$

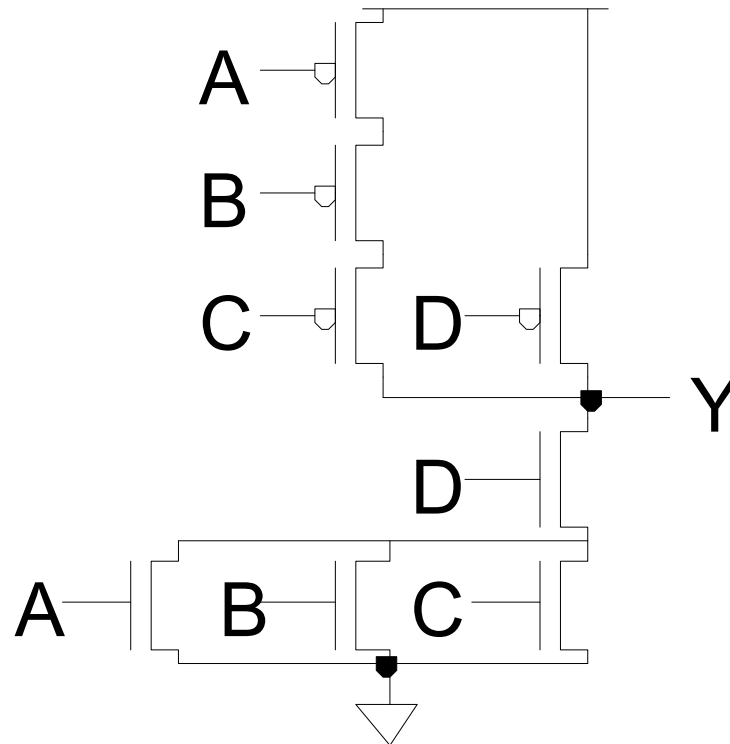

How to optimize the circuit ?

The question of delay, power, space

Two level gate level optimization

Multilevel gate level optimization

Optimization with respect to transistors

Optimization with respect to space in fabrication of Integrated circuits