VLSI LAB REPORT

Name: Anuran Chakraborty

Roll No: 20

Section: A1

Index

Sl. No.	Problem
1	4-to-2 Encoder
2	8-to-3 Encoder
3	Decimal-to-BCD encoder
4	1-to-2 decoder
5	2-to-4 decoder
6	3-to-8 decoder
7	Half Adder
8	Full Adder
9	4-bit Ripple-Carry-Adder
10	BCD Adder
11	Adder/Subtractor circuit

1. Design a 4-to-2 encoder.


Description

An encoder in digital electronics is a one-hot to binary converter. That is, if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. A 4-to-2 encoder has 4 input lines and 2 output lines.

Truth Table

	Inj	out		Out	put
i ₃	\mathbf{i}_2	\mathbf{i}_1	\mathbf{i}_0	01	00
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Block Diagram

 

(a) Using structural modelling.

```
-- Dependencies:
__
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
______
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity foutto2enc str is
    Port ( i : in STD LOGIC VECTOR (3 downto 0);
          o : out STD LOGIC VECTOR (1 downto 0));
end foutto2enc str;
architecture Behavioral of foutto2enc str is
begin
    o(0) \le i(1) \text{ or } i(3);
    o(1) \le i(2) or i(3);
end Behavioral;
(b) Using behavioral modelling using concurrent statements.
-- Company:
-- Engineer:
                 19:38:03 06/07/2020
-- Create Date:
-- Design Name:
-- Module Name:
                 foutto2enc beh - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
```

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

```
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity foutto2enc beh is
    Port ( i : in STD LOGIC VECTOR (3 downto 0);
           o : out STD_LOGIC_VECTOR (1 downto 0));
end foutto2enc beh;
architecture Behavioral of foutto2enc beh is
begin
with i select o<=
    "00" when "0001",
    "01" when "0010",
    "10" when "0100",
    "11" when "1000",
    "ZZ" when others;
end Behavioral;
```

(c) Using behavioral modelling using sequential statements.

-- Company: -- Engineer: -- Create Date: 19:44:18 06/07/2020 -- Design Name: -- Module Name: fourto2enc beh2 - Behavioral -- Project Name: -- Target Devices: -- Tool versions: -- Description: -- Dependencies: __ -- Revision: -- Revision 0.01 - File Created -- Additional Comments: library IEEE; use IEEE.STD LOGIC 1164.ALL;

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity fourto2enc beh2 is
    Port ( i : in STD_LOGIC_VECTOR (3 downto 0);
           o : out STD LOGIC VECTOR (1 downto 0));
end fourto2enc_beh2;
architecture Behavioral of fourto2enc_beh2 is
begin
Process(i)
begin
    case i is
        when "0001" => o<="00";</pre>
        when "0010" => o<="01";</pre>
        when "0100" => o<="10";</pre>
        when "1000" => o<="11";</pre>
        when others => o<="ZZ";
    end case;
end Process;
end Behavioral;
```

2. Design an 8-to-3 encoder.


Description

An encoder in digital electronics is a one-hot to binary converter. That is, if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. An 8-to-3 encoder has 8 input lines and 3 output lines.

Truth Table

			Inj	out				0	utpu	ut
i ₇	\mathbf{i}_6	i 5	i ₄	i ₃	\mathbf{i}_2	\mathbf{i}_1	\mathbf{i}_0	02	01	\mathbf{o}_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Block Diagram

 

(a) Using structural modelling.

-- Company:

-- Engineer:

-- Create Date: 00:29:28 01/27/2020

-- Design Name:

-- Design Name: -- Module Name: eighttothree - Behavioral

-- Project Name:

-- Target Devices:

```
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity eighttothree is
    Port ( i : in STD LOGIC VECTOR (7 downto 0);
           o : out STD LOGIC VECTOR (2 downto 0));
end eighttothree;
architecture Behavioral of eighttothree is
begin
      o(0) \le i(1) or i(3) or i(5) or i(7);
      o(1) \le i(2) or i(3) or i(6) or i(7);
      o(2) \le i(4) or i(5) or i(6) or i(7);
end Behavioral;
      Using behavioral modelling using select statements.
-- Company:
-- Engineer:
                00:47:07 01/27/2020
-- Create Date:
-- Design Name:
                  eighttothree_beh_c - Behavioral
-- Module Name:
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
```

-- Dependencies:

-- Revision 0.01 - File Created

-- Revision:

```
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity eighttothree_beh_c is
    Port ( i : in STD LOGIC VECTOR (7 downto 0);
           o : out STD LOGIC VECTOR (2 downto 0));
end eighttothree beh c;
architecture Behavioral of eighttothree beh c is
begin
with i select o<=
    "000" when "0000001",
    "001" when "0000010",
    "010" when "00000100",
    "011" when "00001000",
    "100" when "00010000",
    "101" when "00100000",
    "110" when "01000000",
    "111" when "10000000",
    "ZZZ" when others ;
end Behavioral;
```

(c) Using behavioral modelling using case statements.

------ Company:
-- Engineer:
--- Create Date: 00:55:27 01/27/2020
-- Design Name:
-- Module Name: eighttothreee_bhe_s - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--- Dependencies:

```
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity eighttothreee bhe s is
    Port ( i : in STD LOGIC VECTOR (7 downto 0);
           o : out STD LOGIC VECTOR (2 downto 0));
end eighttothreee bhe s;
architecture Behavioral of eighttothreee bhe s is
begin
Process(i)
begin
      case i is
            when "00000001" => o<="000";</pre>
            when "00000010" => o<="001";</pre>
            when "00000100" => o<="010";</pre>
            when "00001000" => o<="011";</pre>
            when "00010000" => o<="100";</pre>
            when "00100000" => o<="101";</pre>
            when "01000000" => o<="110";</pre>
            when "10000000" => o<="111";</pre>
            when others => o<="ZZZ";
      end case;
end Process;
end Behavioral;
```

3. Design a decimal-to-BCD encoder.


Description

An encoder in digital electronics is a one-hot to binary converter. That is, if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. A decimal to BCD encoder has 10 input lines and 4 output lines. If i_x is set to 1 then the output is the binary equivalent of x.

Truth Table

				Inj	out						Out	put	
i 9	i ₈	i ₇	\mathbf{i}_6	i ₅	i ₄	i ₃	\mathbf{i}_2	\mathbf{i}_1	\mathbf{i}_0	03	02	01	\mathbf{o}_0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

Block Diagram

 

Code

```
-- Company:
-- Engineer:
-- Create Date:
                   01:21:23 01/27/2020
-- Design Name:
-- Module Name:
                    dectoBCD str - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity dectoBCD str is
    Port ( i : in STD LOGIC VECTOR (9 downto 0);
            o : out STD LOGIC VECTOR (3 downto 0));
end dectoBCD_str;
architecture Behavioral of dectoBCD str is
begin
      \circ (3) <= i(9) or i(8);
      o(2) \leftarrow i(7) \text{ or } i(6) \text{ or } i(5) \text{ or } i(4);
      \circ (1) <= i(7) or i(6) or i(3) or i(2);
      o(0) \leftarrow i(9) \text{ or } i(7) \text{ or } i(5) \text{ or } i(3) \text{ or } i(1);
end Behavioral;
```

4. Design a 1-to-2 decoder.


Description

Decoder is a combinational circuit that has 'n' input lines and maximum of 2ⁿ output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code. A 1-to-2 decoder has 1 input lines and 2 output lines. An enable input is provided to switch the decoder on and off.

Truth Table

Inj	out	Out	tput
e	io	01	00
0	X	0	0
1	0	0	1
1	1	1	0

Gate Diagram

 

(a) Using structural modelling.

```
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity onetotwodecoder is
    Port ( e : in BIT;
           i : in BIT;
           o : out BIT VECTOR (1 downto 0));
end onetotwodecoder;
architecture Behavioral of onetotwodecoder is
begin
o(0) \le e and not(i);
o(1) \le e and i;
end Behavioral;
```

(b) Using behavioral modelling using concurrent statements.

```
-- Company:
-- Engineer:
-- Create Date:
                 00:34:38 02/03/2020
-- Design Name:
-- Module Name:
                 onetotwodecoder2 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity onetotwodecoder2 is
    Port ( e : in BIT;
           i : in BIT;
           o : out BIT VECTOR (1 downto 0));
end onetotwodecoder2;
architecture Behavioral of onetotwodecoder2 is
begin
      with (e & i) select o<=
            "01" when "10",
            "10" when "11",
            "00" when others;
end Behavioral;
```

(c) Using behavioral modelling using sequential statement.

```
______
-- Company:
-- Engineer:
-- Create Date: 00:45:09 02/03/2020
-- Design Name:
-- Module Name:
               onetotwodecoder3 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
____
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity onetotwodecoder3 is
    Port ( e : in STD LOGIC;
           i : in STD LOGIC;
           o : out STD LOGIC VECTOR (1 downto 0));
end onetotwodecoder3;
architecture Behavioral of onetotwodecoder3 is
begin
process(e,i)
begin
      if(e='0') then
            o<="00";
      elsif(i='0') then
            o<="01";
      elsif(i='1') then
            o<="10";
      end if;
end process;
end Behavioral;
```

5. Design a 2-to-4 decoder.


Description

Decoder is a combinational circuit that has 'n' input lines and maximum of 2ⁿ output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code. A 2-to-4 decoder has 2 input lines and 4 output lines. An enable input is provided to switch the decoder on and off.

Truth Table

I	npu	ıt		Out	put	
e	\mathbf{i}_1	\mathbf{i}_0	03	02	01	\mathbf{o}_0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Block Diagram

 

(a) Using structural modelling.

```
-- Company:
-- Engineer:
-- Create Date: 01:09:16 02/03/2020
-- Design Name:
-- Module Name:
                  twotofourdecoder2 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.BIT 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity twotofourdecoder2 is
    Port ( e : in BIT;
           i : in BIT VECTOR (1 downto 0);
           o : out BIT VECTOR (3 downto 0));
end twotofourdecoder2;
architecture Behavioral of twotofourdecoder2 is
begin
      o(0) \le e and not(i(1)) and not(i(0));
      o(1) \le e and not(i(1)) and (i(0));
      o(2) \le and(i(1)) and not (i(0));
      o(3) \le e \text{ and } (i(1)) \text{ and } (i(0));
end Behavioral;
```

(b) Using behavioral modelling sequential statements.

```
-- Company:
-- Engineer:
-- Create Date: 01:48:03 02/03/2020
-- Design Name:
                 twotofourdecoder4 - Behavioral
-- Module Name:
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity twotofourdecoder4 is
    Port ( e : in STD LOGIC;
           i : in STD LOGIC_VECTOR (1 downto 0);
           o : out STD LOGIC VECTOR (3 downto 0));
end twotofourdecoder4;
architecture Behavioral of twotofourdecoder4 is
begin
process(e,i)
begin
      if(e='0') then
            o<="00000";
      elsif(i="00") then
            o<="0001";
      elsif(i="01") then
            o<="0010";
      elsif(i="10") then
            o<="0100";
      elsif(i="11") then
```

```
o<="1000";
end if;
end process;
end Behavioral;</pre>
```

(c) Using behavioral modelling using concurrent statements.

```
-- Company:
-- Engineer:
-- Create Date:
                  01:43:50 02/03/2020
-- Design Name:
-- Module Name: twotofourdecoder3 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity twotofourdecoder3 is
    Port ( e : in STD LOGIC;
           i : in STD LOGIC VECTOR (1 downto 0);
           o : out STD LOGIC VECTOR (3 downto 0));
end twotofourdecoder3;
architecture Behavioral of twotofourdecoder3 is
begin
with (e & i) select o<=
      "0001" when "100",
      "0010" when "101",
      "0100" when "110",
      "1000" when "111",
      "0000" when others;
end Behavioral;
```

6. Design a 3-to-8 decoder.


Description

Decoder is a combinational circuit that has 'n' input lines and maximum of 2ⁿ output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code. A 3-to-8 decoder has 3 input lines and 8 output lines. An enable input is provided to switch the decoder on and off.

Truth Table

	In	put					Out	put			
e	i ₂	\mathbf{i}_1	\mathbf{i}_0	07	06	05	04	03	02	01	00
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Block Diagram

 

(a) Using component instantiate.

```
-- Company:
-- Engineer:
-- Create Date:
                  21:10:22 06/07/2020
-- Design Name:
-- Module Name:
                 threeto8dec comp - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity threeto8dec_comp is
    Port (inp: in STD LOGIC VECTOR (2 downto 0);
                    en : in STD LOGIC;
           op : out STD LOGIC VECTOR (7 downto 0));
end threeto8dec comp;
architecture Behavioral of threeto8dec comp is
component twotofourdecoder4 is
    Port ( e : in STD_LOGIC;
           i : in STD LOGIC VECTOR (1 downto 0);
           o : out STD LOGIC VECTOR (3 downto 0));
end component;
signal notinp:STD LOGIC;
begin
      notinp<=not inp(2);</pre>
      dec1:twotofourdecoder4 port map(inp(2),inp(1 downto 0),op(7 downto 4));
      dec2:twotofourdecoder4 port map(notinp,inp(1 downto 0),op(3 downto 0));
end Behavioral;
```

(b) Using procedural statement.

```
-- Company:
-- Engineer:
-- Create Date:
                 21:23:36 06/07/2020
-- Design Name:
-- Module Name:
                 threeto8dec proc - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity threeto8dec_proc is
    Port (inp: in STD LOGIC VECTOR (2 downto 0);
           op : out STD LOGIC_VECTOR (7 downto 0));
end threeto8dec proc;
architecture Behavioral of threeto8dec proc is
procedure twotofourdecoder3 ( e : in STD LOGIC;
           i : in STD_LOGIC_VECTOR (1 downto 0);
           o : out STD_LOGIC_VECTOR (3 downto 0)) is
begin
      with (e & i) select o:=
            "0001" when "100",
            "0010" when "101",
            "0100" when "110",
            "1000" when "111",
            "0000" when others;
end procedure;
```

7. Design Half Adder using gate level modelling


Description

Half adder is a combinational circuit that adds two bits and produces a sum bit (S) and carry bit (C) as the output. If A and B are the input bits, then sum bit (S) is the X-OR of A and B and the carry bit (C) will be the AND of A and B.

Truth Table

Inj	put	Ou	tput		
\mathbf{i}_1	\mathbf{i}_0	sum	carry		
0	0	0	0		
0	1	1	0		
1	0	1	0		
1	1	0	1		

Block Diagram

 

Code

------ Company:
-- Engineer:
--- Create Date: 23:52:26 02/09/2020
-- Design Name:
-- Module Name: halfadder - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--- Dependencies:
--- Revision:

```
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity halfadder is
    Port ( a : in BIT;
           b : in BIT;
           s : out BIT;
           c : out BIT);
end halfadder;
architecture Behavioral of halfadder is
begin
      s<=a xor b;
      c<=a and b;
end Behavioral;
```

8. Design Full Adder


Description

Full Adder is a combinational circuit which adds three inputs and produces two outputs. The first two inputs are A and B and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM.

Truth Table

	Inj	out	Ou	tput
\mathbf{i}_2	\mathbf{i}_1	\mathbf{i}_0	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Block Diagram

 

(a) Using component instantiate.

- -- Company:
- -- Engineer:

__

- -- Create Date: 23:36:06 02/09/2020
- -- Design Name:
- -- Module Name: fulladder Behavioral
- -- Project Name:

```
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM. VComponents.all;
entity fulladder is
    Port ( x : in BIT;
           y: in BIT;
           z : in BIT;
           s : out BIT;
           c : out BIT);
end fulladder;
architecture Behavioral of fulladder is
component halfadder
    Port ( a : in BIT;
           b : in BIT;
           s : out BIT;
           c : out BIT);
end component;
signal ins:BIT;
signal inc:BIT;
signal inc2:BIT;
begin
      h1:halfadder port map(x,y,ins,inc);
      h2:halfadder port map(z,ins,s,inc2);
      c<=inc2 or inc;</pre>
end Behavioral;
(b) Using function or procedure.
```

28

```
-- Company:
-- Engineer:
-- Create Date: 00:36:27 02/10/2020
-- Design Name:
-- Module Name: fulladder2 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
___
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity fulladder2 is
    Port ( i : in BIT VECTOR (2 downto 0);
           sum : out BIT;
           carry : out BIT);
end fulladder2;
architecture Behavioral of fulladder2 is
procedure halfadder (signal inp:in BIT VECTOR(1 downto 0);
                                       signal s:out BIT;
                                       signal c:out BIT) is
begin
      s<=inp(1) xor inp(0);</pre>
      c \le inp(1) and inp(0);
end procedure;
signal a,b,d: BIT;
signal in1,in2:BIT VECTOR(1 downto 0);
begin
      in1<=i(1 downto 0);
      in2 \le i(2) \& a;
      hal:halfadder(in1,a,b);
      ha2:halfadder(in2,sum,d);
      carry<=b or d;
end Behavioral;
```

9. Design 4-bit Ripple-Carry-Adder


Description

Multiple full adder circuits can be cascaded in parallel to add an N-bit number. For an N- bit parallel adder, there must be N number of full adder circuits. A ripple carry adder is a logic circuit in which the carry-out of each full adder is the carry in of the succeeding next most significant full adder. It is called a ripple carry adder because each carry bit gets rippled into the next stage.

Truth Table

\mathbf{A}_3	\mathbf{A}_{2}	$\mathbf{A}_{\scriptscriptstyle 1}$	\mathbf{A}_{0}	\mathbf{B}_{3}	\mathbf{B}_{2}	B ₁	B _o	$\mathbf{C}_{ ext{out}}$	S_3	S_2	Sı	So
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	1	0	0	0	1	0	1
0	1	0	0	0	1	0	1	0	1	0	0	1
0	1	1	0	1	0	0	0	0	1	1	1	0
1	0	0	1	0	1	1	1	1	0	0	0	0
1	0	1	0	1	0	0	1	1	0	0	1	1
1	1	0	1	1	0	1	0	1	0	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	0

Block Diagram

 

(a) Using generate statement.

-- Company:

-- Engineer:

-- -- Create Date:

20:16:24 06/07/2020

-- Design Name:

-- Description:

-- Module Name: fourbitripple gen - Behavioral

-- Project Name:
-- Target Devices:
-- Tool versions:

```
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity fourbitripple gen is
    Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
    b : in STD_LOGIC_VECTOR (3 downto 0);
           cin : in STD LOGIC;
           s : out STD LOGIC VECTOR (3 downto 0);
           cout : out STD LOGIC);
end fourbitripple gen;
architecture Behavioral of fourbitripple gen is
component fulladder
    Port ( x : in STD LOGIC;
           y : in STD LOGIC;
           z : in STD LOGIC;
           s : out STD LOGIC;
           c : out STD LOGIC);
end component;
signal c:STD LOGIC VECTOR (4 downto 0);
begin
    c(0) \le 0;
    gen1: for i in 0 to 3 generate
        fa:fulladder port map(a(i),b(i),c(i),s(i),c(i+1));
    end generate;
    cout<=c(4);
end Behavioral;
```

(b) Using Loop statement.

```
-- Company:
-- Engineer:
-- Create Date:
                 00:09:50 03/02/2020
-- Design Name:
-- Module Name:
                  fbrcaprocess - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
-- Dependencies:
__
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity fbrcaprocess is
    Port ( a : in BIT VECTOR (3 downto 0);
           b : in BIT VECTOR (3 downto 0);
           sum : out BIT VECTOR (3 downto 0);
           cout : out BIT;
           cin : in BIT);
end fbrcaprocess;
architecture Behavioral of fbrcaprocess is
procedure halfadder(ha,hb:in bit;
                                          hs, hc: out bit) is
begin
      hs:= ha xor hb;
     hc:= ha and hb;
end procedure;
procedure fulladder(fa,fb,fc:in bit;
                                          fss,fcc:out bit) is
variable ints1,ints2,intc1,intc2:bit;
begin
     h1:halfadder(fb,fc,ints1,intc1);
     h2:halfadder(fa,ints1,ints2,intc2);
      fss:=ints2;
```

10. Design BCD Adder.


Description

A BCD adder is used to add two numbers and then get the BCD output instead of the Binary Output.

Truth Table

\mathbf{A}_3	\mathbf{A}_{2}	$\mathbf{A}_{\scriptscriptstyle 1}$	\mathbf{A}_{0}	\mathbf{B}_{3}	\mathbf{B}_{2}	B ₁	B _o	$\mathbf{C}_{\mathrm{out}}$	S_3	S_2	$\mathbf{S}_{\scriptscriptstyle 1}$	So	Decimal
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	0	0	1	1	3
0	1	0	0	0	0	1	1	0	0	1	1	1	7
0	0	0	1	1	0	0	0	0	1	0	0	1	9
0	1	1	0	0	1	0	1	1	0	0	0	1	11
1	0	0	0	0	1	1	0	1	0	1	0	0	14
0	1	1	1	1	0	0	0	1	0	1	0	1	15
1	0	0	1	1	0	0	1	1	1	0	0	0	18

Block Diagram

 

Code

-- Company:

-- Engineer:

__

-- Create Date: 20:06:54 06/07/2020

-- Design Name:

-- Module Name: BCDAdder - Behavioral

-- Project Name:

-- Target Devices:

-- Tool versions:

-- Description:

__

-- Dependencies:

--

```
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM. VComponents.all;
entity BCDAdder is
    Port ( an : in STD LOGIC VECTOR (3 downto 0);
           bn : in STD LOGIC VECTOR (3 downto 0);
           sum : out STD LOGIC VECTOR (3 downto 0);
           k : inout STD LOGIC);
end BCDAdder;
architecture Behavioral of BCDAdder is
component fourbitripple gen is
    Port ( a : in STD LOGIC VECTOR (3 downto 0);
           b : in STD LOGIC VECTOR (3 downto 0);
           cin : in STD LOGIC;
           s : out STD LOGIC VECTOR (3 downto 0);
           cout : out STD LOGIC);
end component;
signal binarySum: STD LOGIC VECTOR (3 downto 0);
signal carry: STD LOGIC;
signal condition: STD LOGIC;
signal toAdd: STD LOGIC VECTOR (3 downto 0);
signal nouse: STD LOGIC;
begin
      rc1:fourbitripple gen port map(an,bn,'0',binarySum,carry);
      condition <= carry or (binarySum(3) and binarySum(2)) or (binarySum(3))
and binarySum(1));
      Process (toAdd, condition)
      begin
            if(condition='0') then
                  toAdd<="0000";
            elsif(condition='1') then
                  toAdd<="0110";
            end if;
      end process:
      rc2:fourbitripple gen port map(binarySum, toAdd, '0', sum, k);
end Behavioral;
```

11. Design Adder/Subtractor circuit.


Description

A Binary Adder-Subtractor is one which is capable of both addition and subtraction of binary numbers in one circuit itself. The operation being performed depends upon the binary value the control signal holds. It is one of the components of the ALU (Arithmetic Logic Unit).

Truth Table

Cin	\mathbf{A}_3	\mathbf{A}_{2}	$\mathbf{A}_{\scriptscriptstyle 1}$	\mathbf{A}_{0}	\mathbf{B}_{3}	\mathbf{B}_{2}	B ₁	\mathbf{B}_{0}	$\mathbf{C}_{ ext{out}}$	S_3	S_2	Sı	So
0	0	0	0	1	0	0	1	0	0	0	0	1	1
1	0	0	0	1	0	0	1	0	0	0	1	0	1
0	1	0	0	0	0	1	0	1	0	1	1	0	1
1	1	0	0	0	0	1	0	1	0	0	0	1	1
0	0	1	1	1	1	0	1	0	1	0	0	0	1
1	0	1	1	1	1	0	1	0	0	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	0	0	0
1	1	1	1	1	1	1	1	1	0	0	0	0	0

Block Diagram

 

Code

-- Company:

-- Engineer:

-- Create Date: 00:09:23 02/17/2020

-- Design Name:

-- Module Name: addersub - Behavioral

-- Project Name:

-- Target Devices:

```
-- Tool versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity addersub is
    Port ( a : in BIT_VECTOR (3 downto 0);
           b : in BIT VECTOR (3 downto 0);
           cin : in BIT;
           s : out BIT VECTOR (3 downto 0);
           cout : out BIT);
end addersub;
architecture Behavioral of addersub is
component fulladder
    Port ( x : in BIT;
           y : in BIT;
           z : in BIT;
           s : out BIT;
           c : out BIT);
end component;
signal c:BIT VECTOR (4 downto 0);
signal inputb:BIT VECTOR (3 downto 0);
begin
      inputb<=b when cin='0' else not(b);</pre>
      c(0) \le cin;
      gen1:for i in 0 to 3 generate
            fa:fulladder port map(a(i),inputb(i),c(i),s(i),c(i+1));
      cout\leq='0' when cin='1' and c(4)='1' else c(4);
end Behavioral:
```